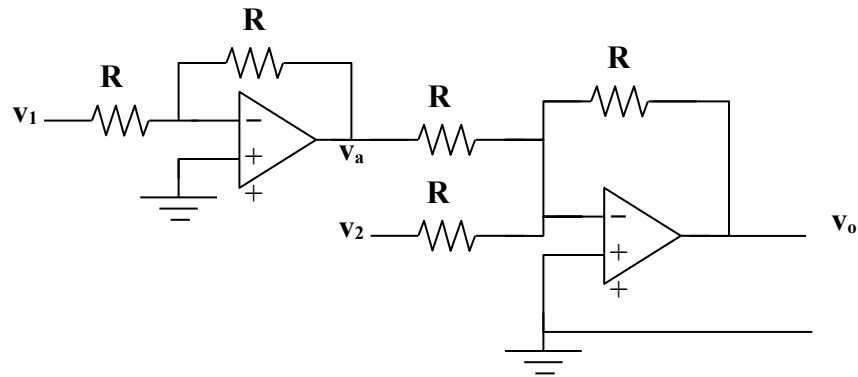


Chapter 5, Solution 51.

We achieve this by cascading an inverting amplifier and two-input inverting summer as shown below:



Verify:

$$v_o = -v_a - v_2$$

But

$$v_a = -v_1. \text{ Hence}$$

$$v_o = v_1 - v_2.$$