

### Chapter 7, Problem 65.

If the input pulse in Fig. 7.130 (a) is applied to the circuit in Fig. 7.130 (b), determine the response  $i(t)$ .

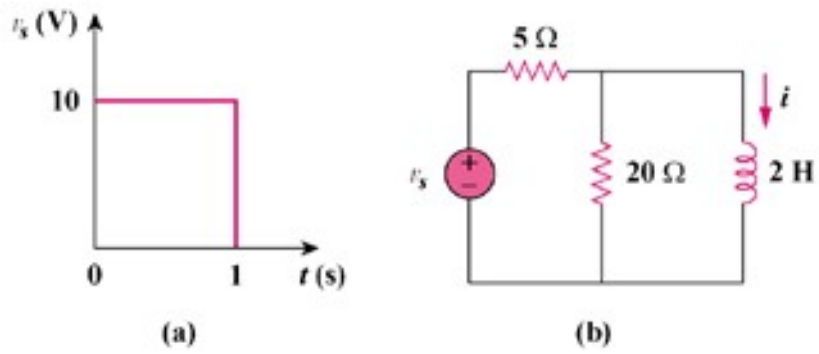


Figure 7.130  
For Prob. 7.65.