

**Chapter 5, Problem 25.**

Calculate  $v_o$  in the op amp circuit of Fig. 5.63.

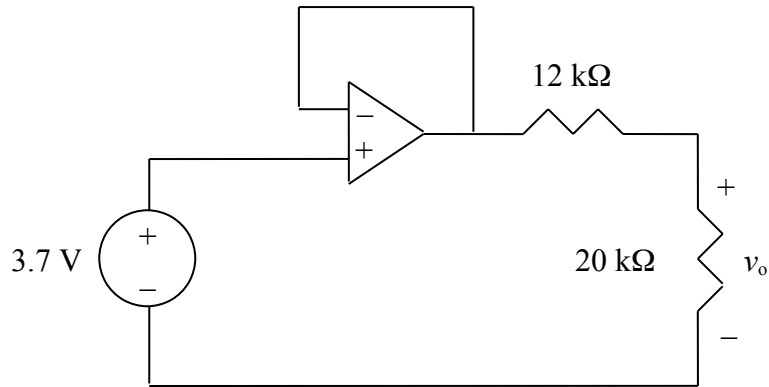


Figure 5.63  
For Prob. 5.25.