

Chapter 5, Problem 19

Determine i_o in the circuit of Fig. 5.58.

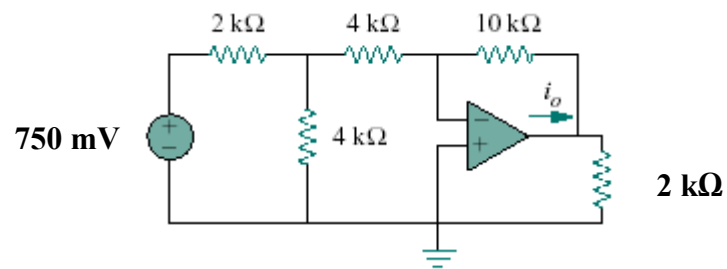


Figure 5.58
For Prob. 5.19.