Chapter 7, Solution 8.

(a)
$$\tau = RC = \frac{1}{4}$$

$$-i = C \frac{dv}{dt}$$

$$-0.2e^{-4t} = C(10)(-4)e^{-4t} \longrightarrow C = 5 \text{ mF}$$

$$R = \frac{1}{4C} = 50 \Omega$$

(b)
$$\tau = RC = \frac{1}{4} = 0.25 \text{ s}$$

(c)
$$W_C(0) = \frac{1}{2}CV_0^2 = \frac{1}{2}(5 \times 10^{-3})(100) = 250 \text{ mJ}$$

(d)
$$w_{R} = \frac{1}{2} \times \frac{1}{2} CV_{0}^{2} = \frac{1}{2} CV_{0}^{2} \left(1 - e^{-2t_{0}/\tau}\right)$$

$$0.5 = 1 - e^{-8t_{0}} \longrightarrow e^{-8t_{0}} = \frac{1}{2}$$
or
$$e^{8t_{0}} = 2$$

$$t_{0} = \frac{1}{8} \ln(2) = 86.6 \text{ ms}$$