

Chapter 10, Problem 17.

By nodal analysis, obtain current \mathbf{I}_o in the circuit in Fig. 10.66.

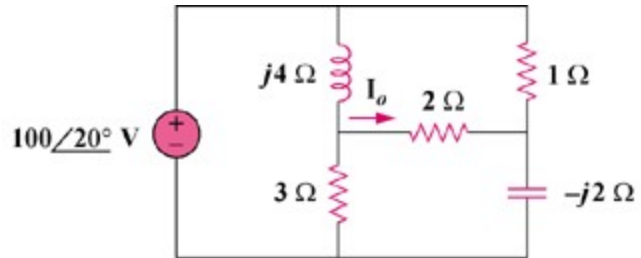


Figure 10.66
For Prob. 10.17.