

Chapter 10, Problem 23.

Using nodal analysis obtain \mathbf{V} in the circuit shown in Fig. 10.72.

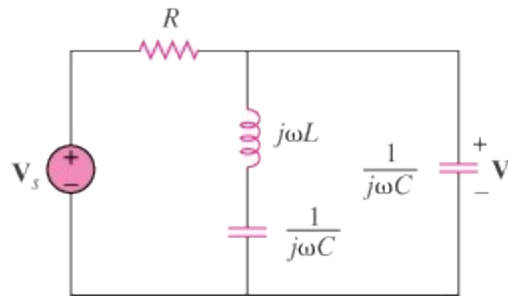


Figure 10.72
For Prob. 10.23.