

Chapter 5, Solution 48.

The circuit in Fig. 5.80 is a differential amplifier driven by a bridge. Find v_o .

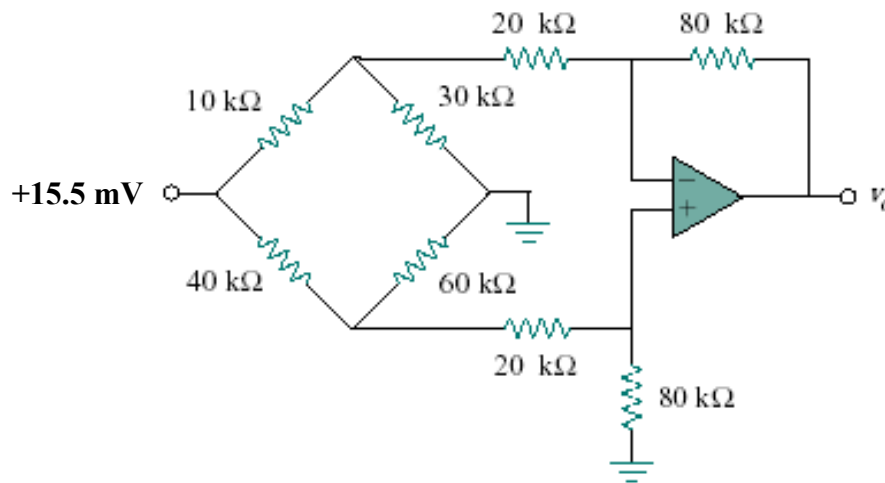


Figure 5.80
For Prob. 5.48.

Solution

We can break this problem up into parts. The 15.5 mV source separates the lower circuit from the upper. In addition, there is no current flowing into the input of the op amp which means we now have the 40-kohm resistor in series with a parallel combination of the 60-kohm resistor and the equivalent 100-kohm resistor.

$$\text{Thus, } 40\text{k} + (60 \times 100\text{k}) / (160) = 77.5\text{k}$$

which leads to the current flowing through this part of the circuit,

$$i = 15.5 \text{ m} / 77.5\text{k} = 200 \times 10^{-9} \text{ A}$$

The voltage across the 60k and equivalent 100k is equal to,

$$v = i \times 37.5\text{k} = 7.5 \text{ mV}$$

We can now calculate the voltage across the 80-kohm resistor.

$$v_{80} = 0.8 \times 7.5 \text{ m} = 6 \text{ mV}$$

which is also the voltage at both inputs of the op amp and the voltage between the 20-kohm and 80-kohm resistors in the upper circuit. Let v_1 be the voltage to the

left of the 20-kohm resistor of the upper circuit and we can write a node equation at that node.

$$(v_1 - 15.5\text{m})/(10\text{k}) + v_1/30\text{k} + (v_1 - 6\text{m})/20\text{k} = 0$$

or $6v_1 - 93 + 2v_1 + 3v_1 - 18 = 0$ or $v_1 = 10.091 \text{ mV}$.

The current through the 20k-ohm resistor, left to right, is,

$$i_{20} = (10.091\text{m} - 6\text{m})/20\text{k} = 204.55 \times 10^{-9} \text{ A}$$

thus, $v_o = 6\text{m} - 204.55 \times 10^{-9} \times 80\text{k} = \mathbf{-10.364 \text{ mV}}$.