

### Chapter 10, Solution 4.

Compute  $v_o(t)$  in the circuit of Fig. 10.53.


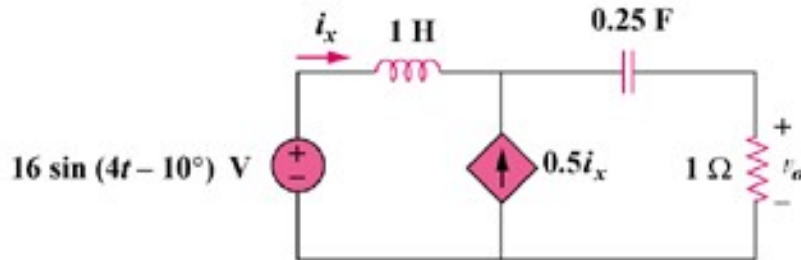


Figure 10.53  
For Prob. 10.4.
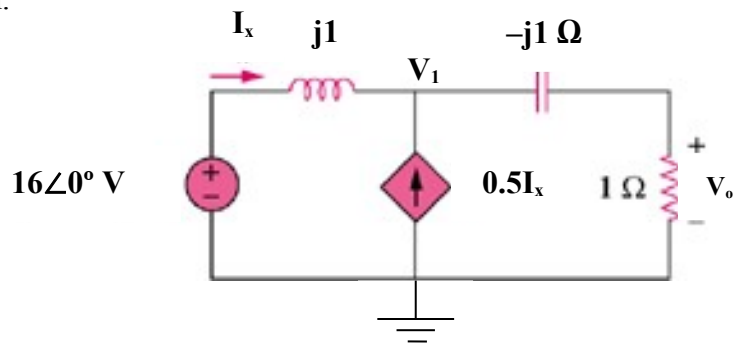
### Solution

Step 1. Convert the circuit into the frequency domain and solve for the node voltage,  $V_1$ , using analysis. Then find the current  $I_C = V_1/[1+(1/(j4 \times 0.25))]$  which then produces  $V_o = 1 \times I_C$ . Finally, convert the capacitor voltage back into the time domain.



Note that we represented  $16\sin(4t-10^\circ)$  volts by  $16\angle 0^\circ$  V. That will make our calculations easier and all we have to do is to offset our answer by a  $-10^\circ$ .

Our node equation is  $[(V_1-16)/j] - (0.5I_x) + [(V_1-0)/(1-j)] = 0$ . We have two unknowns, therefore we need a constraint equation.  $I_x = [(16-V_1)/j] = j(V_1-16)$ . Once we have  $V_1$ , we can find  $I_o = V_1/(1-j)$  and  $V_o = 1 \times I_o$ .

Step 2. Now all we need to do is to solve our equations.

$$[(V_1-16)/j] - [0.5j(V_1-16)] + [(V_1-0)/(1-j)] = [-j-j0.5+0.5+j0.5]V_1 + j16+j8 = 0 \text{ or}$$

$$[0.5-j]V_1 = -j24 \text{ or } V_1 = j24/(-0.5+j) = (24\angle 90^\circ)/(1.118\angle 116.57^\circ) \\ = 21.47\angle -26.57^\circ \text{ V.}$$

$$\text{Finally, } I_x = V_1/(1-j) = (21.47\angle -26.57^\circ)(0.7071\angle 45^\circ) = 15.181\angle 18.43^\circ \text{ A and } V_o \\ = 1xI_o = 15.181\angle 18.43^\circ \text{ V or}$$

$$v_o(t) = 15.181\sin(4t-10^\circ+18.43^\circ) = \mathbf{15.181\sin(4t-8.43^\circ) \text{ volts.}}$$