

### Chapter 5, Problem 58

Calculate  $i_o$  in the op amp circuit of Fig. 5.85.

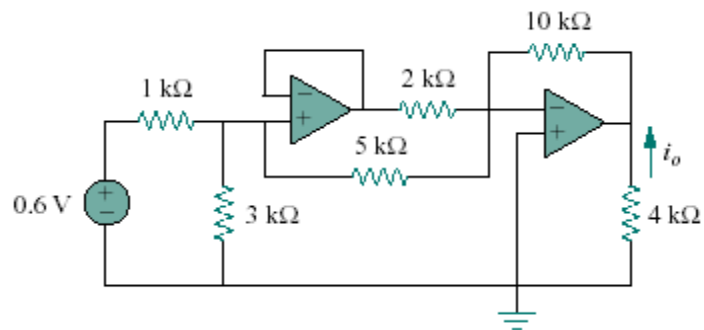


Figure 5.85  
For Prob. 5.58.