

Chapter 5, Problem 49

Design a difference amplifier to have a gain of 4 and a common mode input resistance of $20\text{ k}\Omega$ at each input.