

**Chapter 11, Problem 58.**

Obtain the complex power delivered to the 10-k $\Omega$  resistor in Fig. 11.77 below.

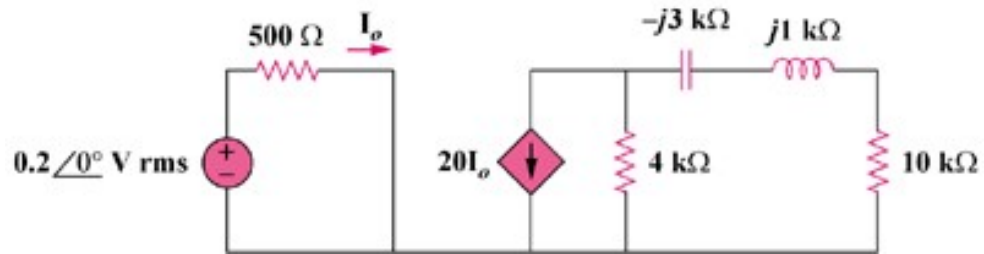


Figure 11.77  
For Prob. 11.58.