

**Chapter 9, Problem 82.**

A capacitance bridge balances when  $R_1 = 100\ \Omega$ ,  $R_2 = 2\ \text{k}\Omega$ , and  $C_s = 40\ \mu\text{F}$ .  
What is  $C_x$ , the capacitance of the capacitor under test?