

Chapter 10, Problem 38.

Using mesh analysis, obtain \mathbf{I}_o in the circuit shown in Fig. 10.83.

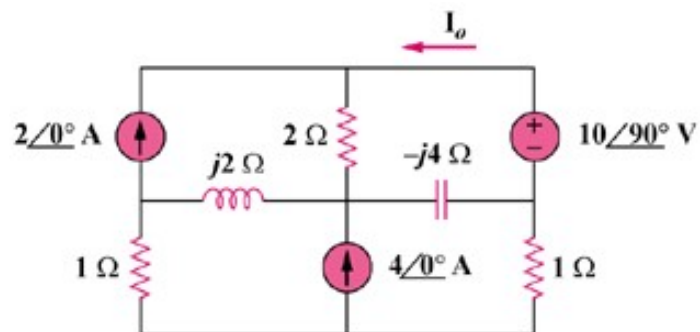


Figure 10.83
For Prob. 10.38.