

Chapter 5, Problem 69

Repeat the previous problem if $R_f = 10\text{ k}\Omega$.

Chapter 5, Problem 69.

Find v_o in the circuit in Fig. 5.93, assuming that $R_f = \infty$ (open circuit).

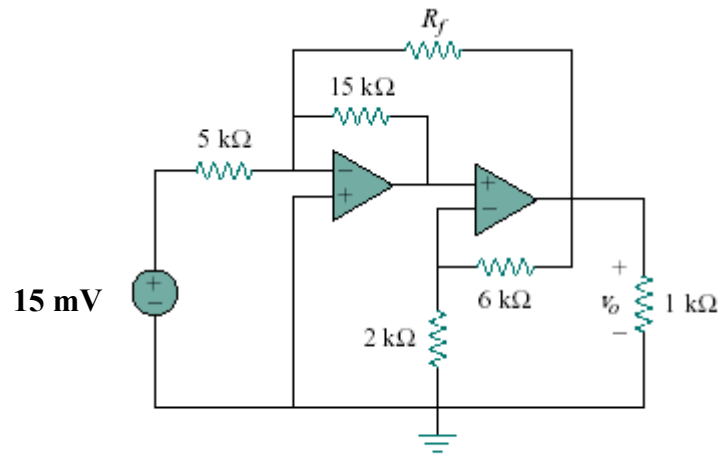


Figure 5.93
For Prob. 5.68 and 5.69.