

Chapter 10, Problem 52.

Use the method of source transformation to find \mathbf{I}_x in the circuit of Fig. 10.96.

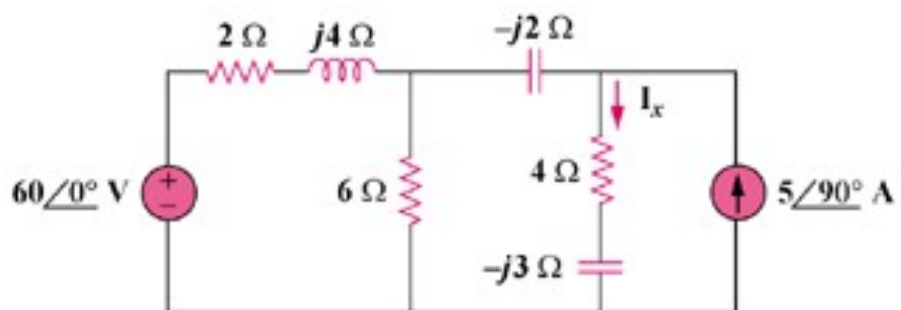


Figure 10.96
For Prob. 10.52.