

**Chapter 9, Problem 72.**

Calculate the value of  $\mathbf{Z}_{ab}$  in the network of Fig. 9.79.

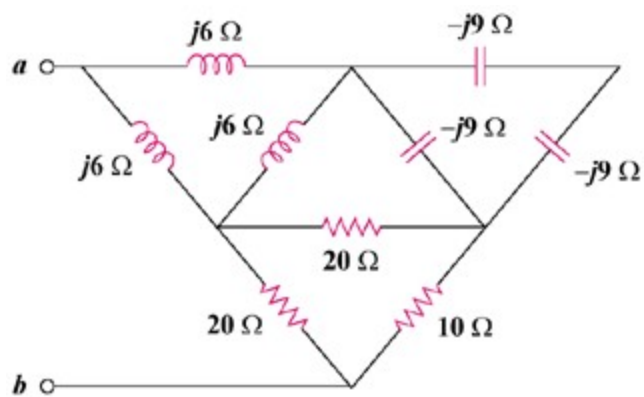


Figure 9.79  
For Prob. 9.72.