

Chapter 10, Solution 58.

For the circuit depicted in Fig. 10.101, find the Thevenin equivalent circuit at terminals a - b .


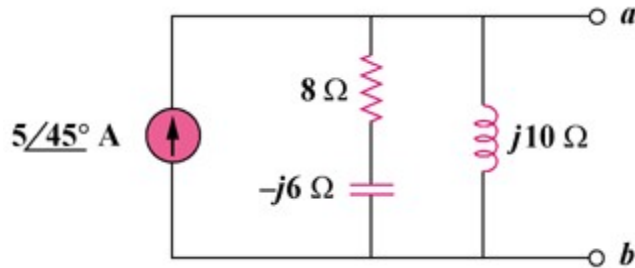


Figure 10.101
For Prob. 10.58.


Solution

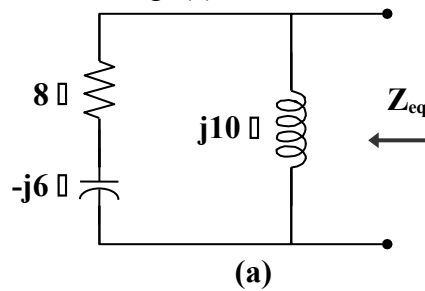Consider the circuit in Fig. (a) to find Z_{eq} .



$$Z_{eq} = j10 \parallel (8 - j6) = \frac{(j10)(8 - j6)}{8 + j4} = 5(2 + j) \\ = 11.18 \angle 26.56^\circ \Omega$$

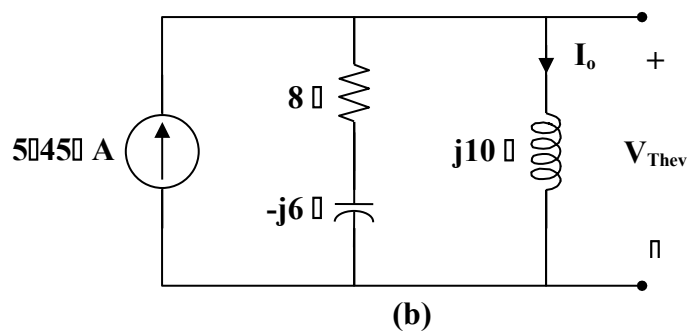Consider the circuit in Fig. (b) to find V_{Th} .



$$\mathbf{I}_o = \frac{8 - j6}{8 - j6 + j10} (5 \angle 45^\circ) = \frac{4 - j3}{4 + j2} (5 \angle 45^\circ)$$

$$\begin{aligned} \mathbf{V}_{Thev} = j10 \mathbf{I}_o &= \frac{(j10)(4 - j3)(5 \angle 45^\circ)}{(2)(2 + j)} \\ &= 55.9 \angle 71.56^\circ \text{ V} \end{aligned}$$