

### Chapter 11, Solution 85.

A regular household system of a single-phase three-wire allows the operation of both 120-V and 240-V, 60-Hz appliances. The household circuit is modeled as shown in Fig. 11.96. Calculate: (a) the currents  $I_1$ ,  $I_2$ , and  $I_n$ , (b) the total complex power supplied, (c) the overall power factor of the circuit.


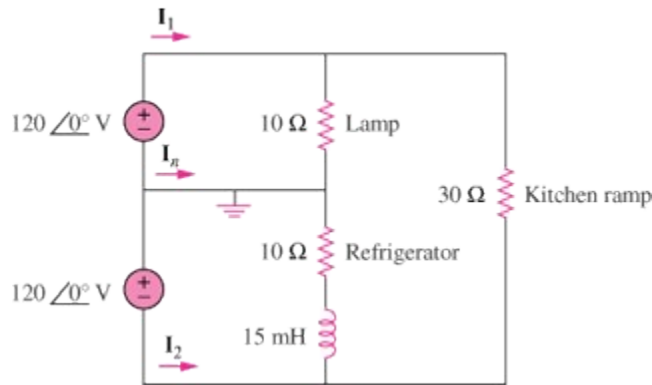


Figure 11.96  
For Prob. 11.85.

### Solution

(a)  $15 \text{ mH} \longrightarrow j2\pi \times 60 \times 15 \times 10^{-3} = j5.655$

We apply mesh analysis as shown below.

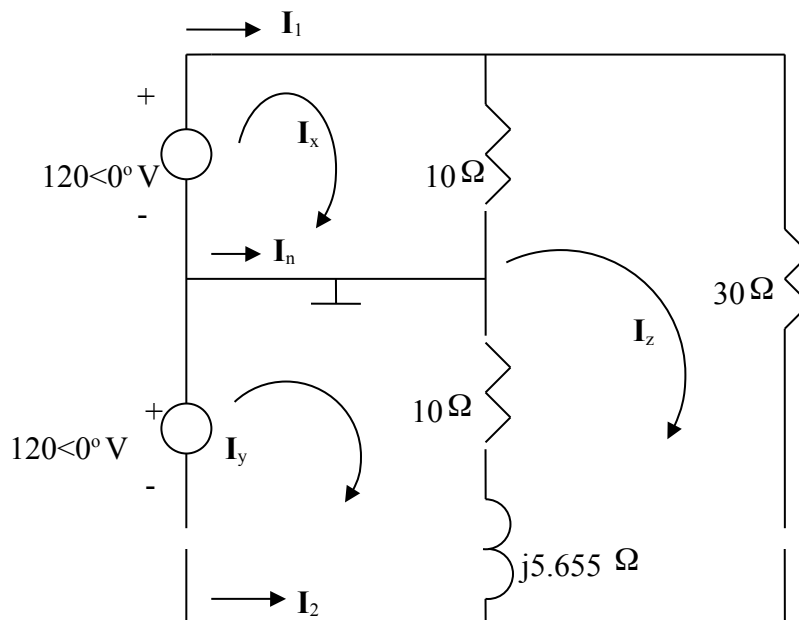

For mesh x,

$$120 = 10 \mathbf{I}_x - 10 \mathbf{I}_z \quad (1)$$

For mesh y,

$$120 = (10+j5.655) \mathbf{I}_y - (10+j5.655) \mathbf{I}_z \quad (2)$$

For mesh z,

$$0 = -10 \mathbf{I}_x - (10+j5.655) \mathbf{I}_y + (50+j5.655) \mathbf{I}_z \quad (3)$$

Solving (1) to (3) gives

$$\mathbf{I}_x = 20, \mathbf{I}_y = 17.09 - j5.142, \mathbf{I}_z = 8$$

Thus,

$$\mathbf{I}_1 = \mathbf{I}_x = \mathbf{20 \text{ A}}$$

$$\mathbf{I}_2 = -\mathbf{I}_y = -17.09 + j5.142 = \frac{17.85 \angle 163.26^\circ \text{ A}}{1} = 17.85 \angle 163.26^\circ \text{ A}$$

$$\mathbf{I}_n = \mathbf{I}_y - \mathbf{I}_x = -2.91 - j5.142 = \frac{5.907 \angle -119.5^\circ \text{ A}}{1} = 5.907 \angle -119.5^\circ \text{ A}$$

$$(b) \overline{S}_1 = (120) \mathbf{I}_x^\bullet = 120 \times 20 = 2400, \quad \overline{S}_2 = (120) \mathbf{I}_y^\bullet = 2051 + j617$$

$$\overline{S} = \overline{S}_1 + \overline{S}_2 = \underline{[4.451 + j0.617] \text{ kVA}}$$

$$(c) \text{ pf} = P/S = 4451/4494 = \mathbf{0.9904} \text{ (lagging)}$$