


Chapter 10, Solution 51.

There are many ways to create this problem, here is one possible solution. Let $V_1 = 40\angle 30^\circ$ V, $X_L = 10\ \Omega$, $X_C = 20\ \Omega$, $R_1 = R_2 = 80\ \Omega$, and $V_2 = 50$ V.

If we let the voltage across the capacitor be equal to V_x , then

$$\mathbf{I}_o = [\mathbf{V}_x/(-j20)] + [(\mathbf{V}_x - 50)/80] = (0.0125 + j0.05)\mathbf{V}_x - 0.625 = (0.051539\angle 75.96^\circ)\mathbf{V}_x - 0.625.$$

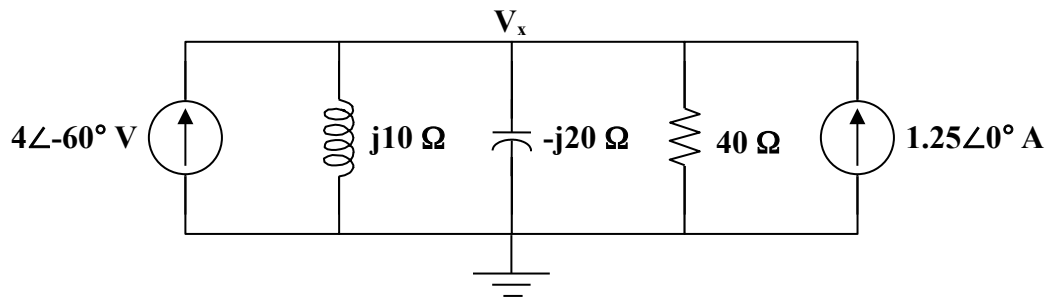The following circuit is obtained by transforming the voltage sources.



$$\begin{aligned}\mathbf{V}_x &= (4\angle -60^\circ + 1.25)/(-j0.1 + j0.05 + 0.025) = (2 - j3.4641 + 1.25)/(0.025 - j0.05) \\ &= (3.25 - j3.4641)/(0.025 - j0.05) = (4.75\angle -46.826^\circ)/(0.055902\angle -63.435^\circ) \\ &= 84.97\angle 16.609^\circ \text{ V.}\end{aligned}$$

Therefore,

$$\begin{aligned}\mathbf{I}_o &= (0.051539\angle 75.96^\circ)(84.97\angle 16.609^\circ) - 0.625 = 4.3793\angle 92.569^\circ - 0.625 \\ &= -0.196291 + j4.3749 - 0.625 = -0.821291 + j4.3749 = \mathbf{4.451\angle 100.63^\circ \text{ A.}}\end{aligned}$$