

Chapter 10, Problem 96.

Refer to the oscillator in Fig. 10.137.

(a) Show that

$$(V_2/V_o) = 1/[3 + j(\omega L/R - R/\omega L)]$$

(b) Determine the oscillation frequency f_o .

(c) Obtain the relationship between R_1 and R_2 in order for oscillation to occur.

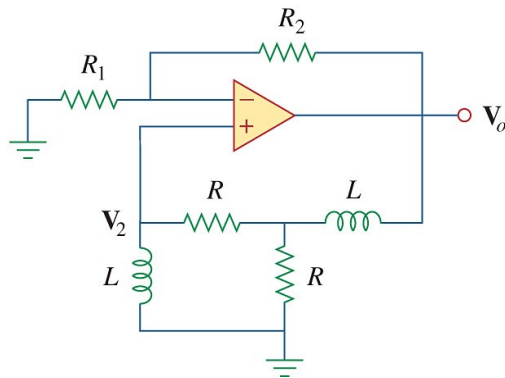


Figure 10.137
For Prob. 10.96.