Chapter 10, Problem 82.

Solve Prob. 10.19 using *PSpice*.
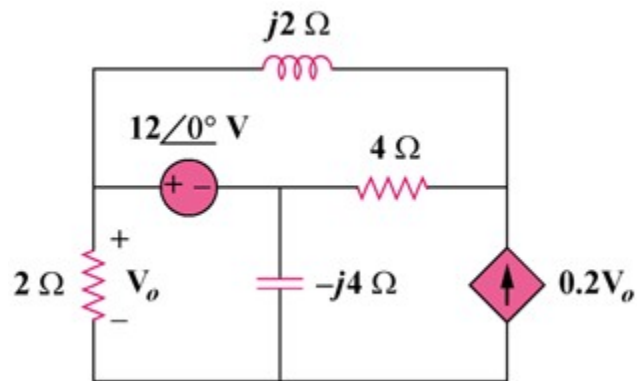
Chapter 10, Problem 19.

Obtain $\mathbf{V}_o$ in Fig. 10.68 using nodal analysis.

Figure 10.68
For Prob. 10.82.